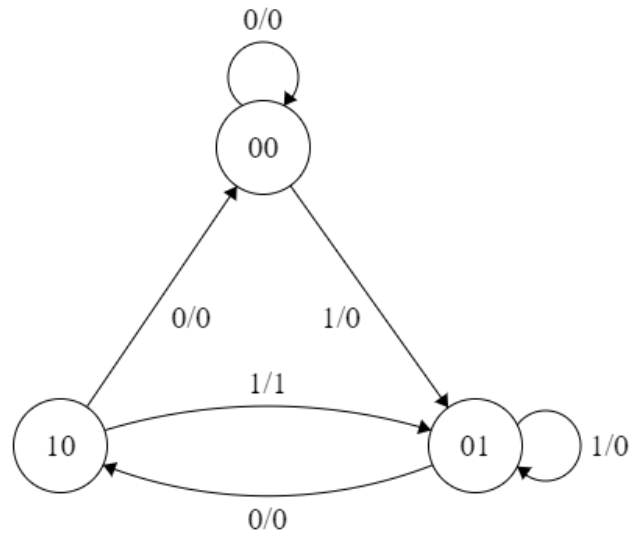


### Sequential Circuit Using State Diagram



Truth Table:

Q <sub>1</sub>	Q <sub>2</sub>	x	Q <sub>1</sub> <sup>+</sup>	Q <sub>2</sub> <sup>+</sup>	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	x(1)	x(0)	x(0)
1	1	1	x(0)	x(1)	x(1)

K-Map  $Q_1^+$ :

			Q2	
	0	0	0	1
Q1	0	0	x	x
		x		

$$Q_1^+ = Q_2x' \quad (6 = 1; 7 = 0)$$

K-Map  $Q_2^+$ :

			Q2	
	0	1	1	0
Q1	0	1	x	x
		x		

$$Q_2^+ = x \quad (6 = 0; 7 = 1)$$

K-Map  $Q_3^+$ :

			Q2	
	0	0	0	0
Q1	0	1	x	x
		x		

$$Q_3^+ = Q_1x$$

This circuit is self-correcting: the forbidden state (11) lead into two authorized states (10) and (01).

Truth Table:

Q <sub>1</sub>	Q <sub>2</sub>	x	Q <sub>1</sub> <sup>+</sup>	Q <sub>2</sub> <sup>+</sup>	y	T <sub>1</sub>	T <sub>2</sub>	z
0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1	0
0	1	0	1	0	0	1	1	0
0	1	1	0	1	0	0	0	0
1	0	0	0	0	0	1	0	0
1	0	1	0	1	1	1	1	1
1	1	0	x(1)	x(0)	x(0)	x(1)	x(1)	x(0)
1	1	1	x(0)	x(1)	x(1)	x(1)	x(0)	x(1)

K-Map T<sub>1</sub>:

		Q <sub>2</sub>	
	0	0	1
Q <sub>1</sub>	1	1	x
		x	

$$T_1 = Q_1 + Q_2x' \quad (\text{both } x\text{'s in } T_1 \text{ become } 1\text{'s})$$

K-Map T<sub>2</sub>:

		Q <sub>2</sub>	
	0	1	1
Q <sub>1</sub>	1	1	x
		x	

$$T_2 = Q_2'x + Q_2x' \quad (6 \text{ in } T_2 = 1; 7 \text{ in } T_2 = 0)$$

K-Map of z is unnecessary. The values of z are identical to those in y including the x's.

The forbidden state (11) leads into itself (11) in row 7 but it does lead into authorized state (10) in row 8.